

# TRANSISTORS REPLACE FOUR-LAYER DEVICES

Economy, parameter control, packaging—these factors may dictate the substitution of a transistor model for a four-layer device.

WESLEY A. VINCENT, MOTOROLA, INC.

Variouly named Shockley diode, reverse-blocking thyristor or silicon unilateral switch, the four-layer diode exhibits a V-I response that travels through a negative resistance region. This characteristic is explained easily by a transistor model that indicates that a similar device can be constructed with two transistors and a resistor.

The two transistors and a resistor may:

- Cost less than a four-layer semiconductor.
- Permit better parameter control.
- Be better adapted to a hybrid package since transistors now are available in chip form.

The transistor-resistor configuration gives the designer a wide range of switching voltage and holding currents. Further, the shunt resistors suppress the tendency toward premature switching from high di/dt

to bulk rate effects. This concept is generally applied to the thyristor family, but can be extended to other devices such as the unijunction transistor (UJT)—simply add two resistors.

## UJT Equivalent

Either circuit in Fig. 1 represents the equivalent of a UJT. Neither appears to have any advantage over the other. Resistors  $R_{B1}$  and  $R_{B2}$  represent the interbase resistance and establish the peak point voltage. By proper selection, the designer can establish the required level for his needs.

## Application

A p-base UJT relaxation oscillator is illustrated in Fig. 2. The oscillator frequency is determined by the

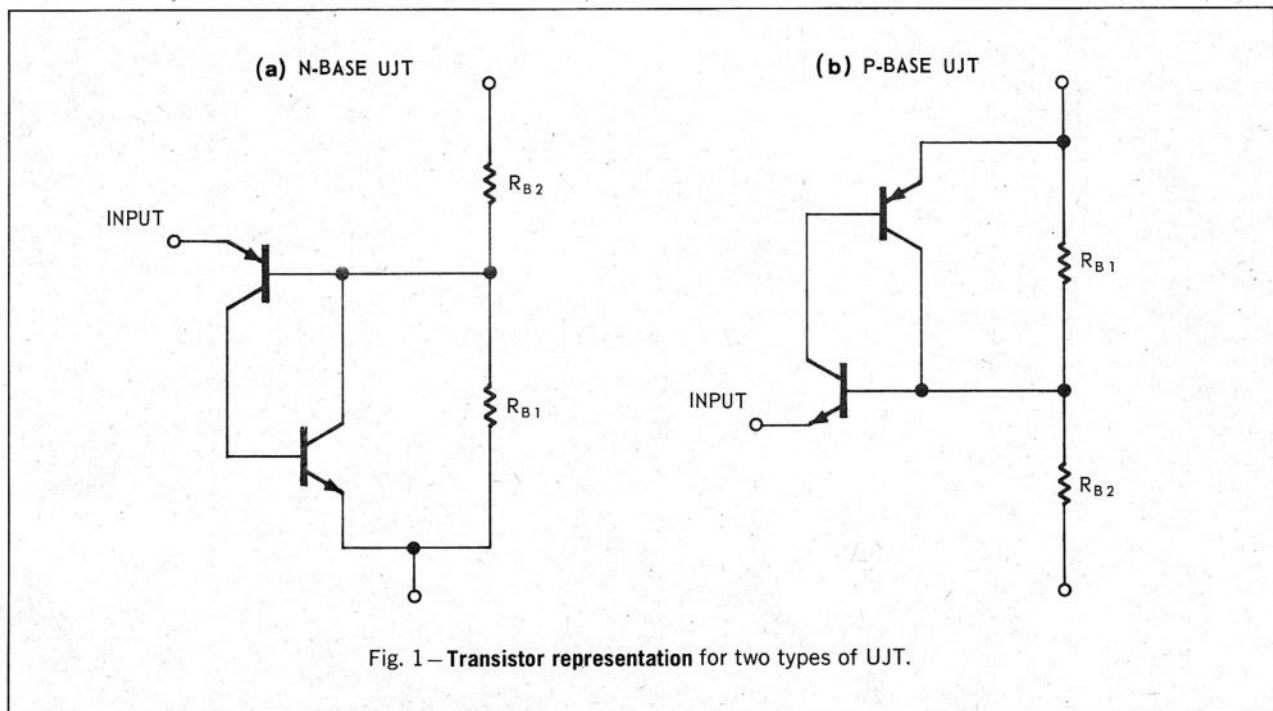


Fig. 1—Transistor representation for two types of UJT.

(Continued)

## Transistors (Cont'd)

time constant of  $R_1 C_1$ , and the discharge current through the emitter is limited by  $R_2$ . Resistor  $R_3$  is selected for temperature compensation and develops a positive pulse at base-2 during operation.

Interbase resistance ratio (intrinsic standoff ratio) combined with emitter diode drop determine the firing point. Depending on the UJT construction, one of two mechanisms occurs during firing. In conventional "bar", "cube" or "planar" n-base UJT, the resistance between the emitter and base-1 is decreased by the carriers injected across the junction. This is known as conductivity modulation of the bulk silicon. In the recently introduced p-base UJT, the basic mechanism is because of the low-impedance pnpn, four-layer action.


In Fig 2b, the operation of the transistor equivalent

is similar and depends on the pnpn performance for its regenerative action. Voltage divider  $R_{B1}$ ,  $R_{B2}$ ,  $R_2$  and the base-emitter drop of  $Q_2$  establish the firing point. During firing,  $C_1$  is discharged through the low impedance of the transistor equivalent.


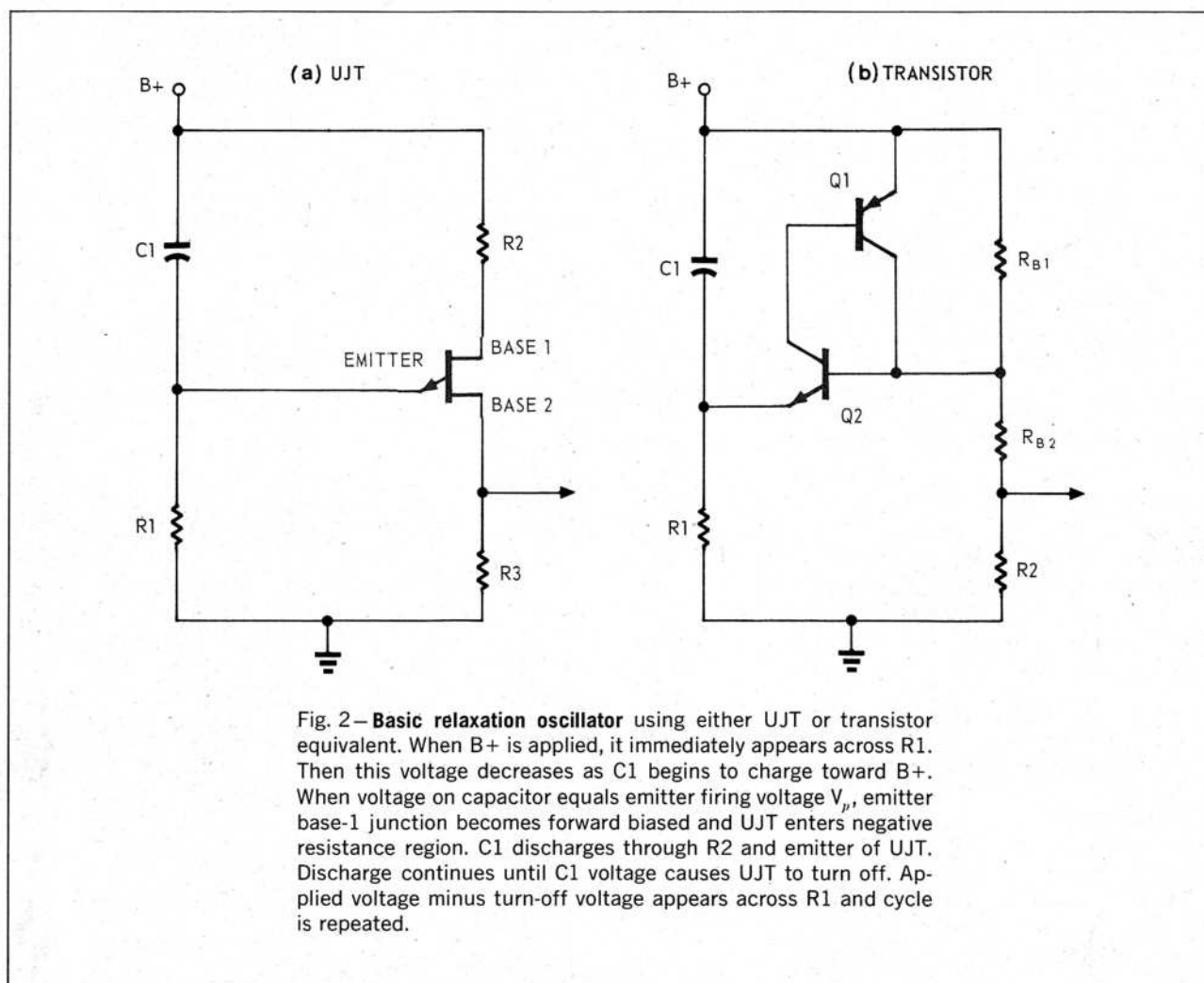
### Test Results

Test results for a 1000-Hz oscillator using the transistor model are plotted in Fig. 3. The pnp and npn transistors are types 2N2907 and 2N2222, respectively, with an applied voltage of +10V, regulated. Similar results were obtained with other silicon transistors.

For the tests, frequency-determining components ( $R_1$  and  $C_1$ ) remained outside the temperature chamber or subject to room ambient temperature. Thus, all


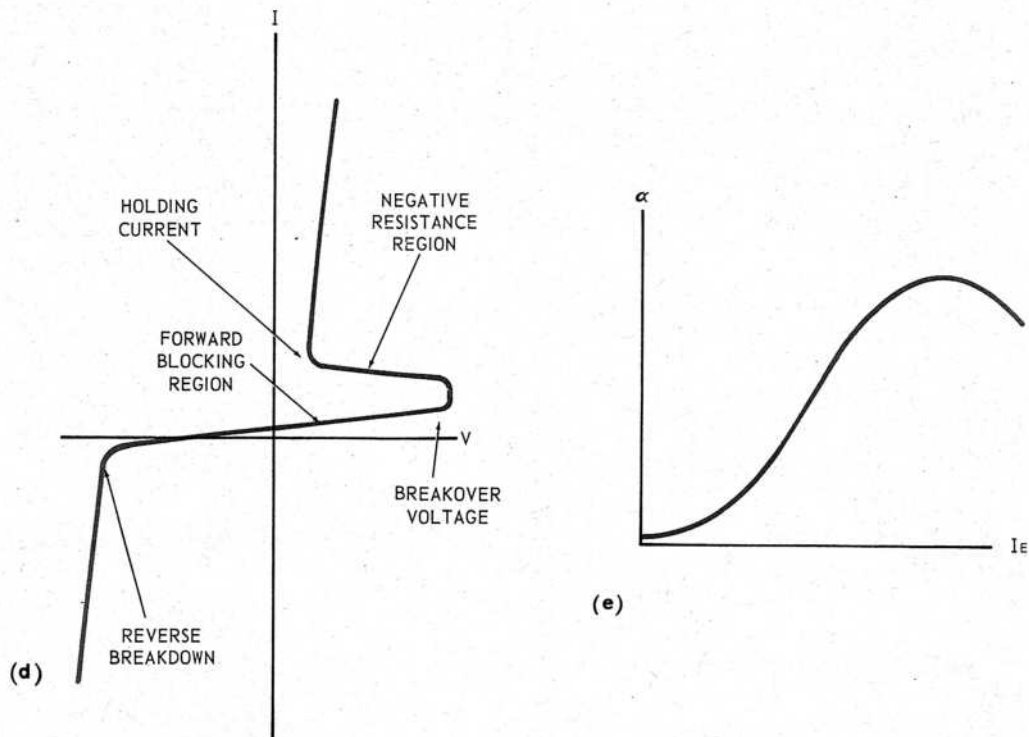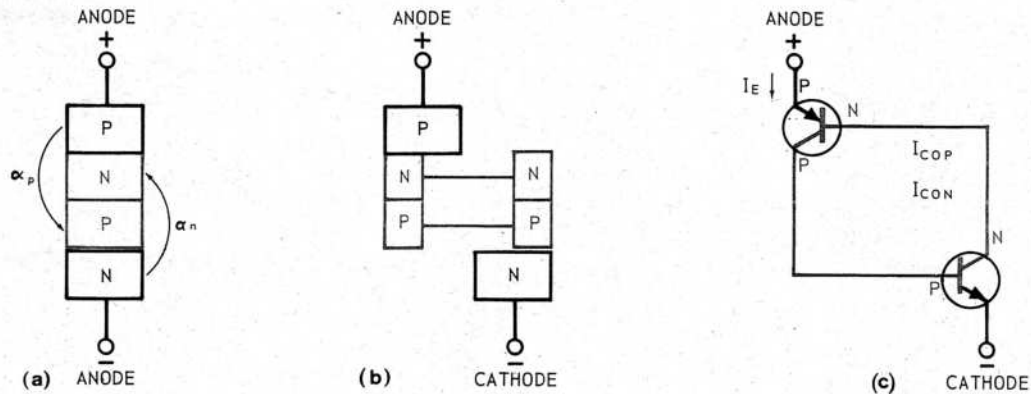
## TRANSISTOR MODEL DEVELOPMENT OF FOUR-LAYER DIODE



Classical diagrams (a) to (c) show the evolution of a transistor version of four-layer diode. Unusual characteristic response curve (d) is caused by variability of multiplication factor,  $M$  and current gains  $\alpha_p$  and  $\alpha_n$ .

Mathematically, terminal current  $I_E$  may be expressed as:

$$I_E = \frac{I_{cop} + I_{con}}{1 - (M_p \alpha_p + M_n \alpha_n)} \quad (1)$$

where p and n subscripts refer to pnp or npn devices and  $I_{co}$  represents collector-to-base leakage currents. Multiplication factor,  $M$ , accounts for carriers created by impact ionization in reverse-biased junction.

Practically,  $M_p$  and  $M_n$  can be assumed equal, designated as  $M$ . Leverages are combined and (1) becomes:

$$I_E = \frac{I_{co}}{1 - M(\alpha_p + \alpha_n)} \quad (2)$$

At less than breakover voltage, only small leakage cur-

rent flows. Current gain parameters are much less than 1,  $M$  is unity. As forward voltage is continually increased the condition occurs where  $M(\alpha_p + \alpha_n) = 1$ . Current then increases sharply over previous small leakage current. The voltage at this point is termed breakover voltage.  $M$  exceeds unity, since avalanche breakdown occurs in reverse-biased junction.

Interaction between  $M$ ,  $\alpha_p$  and  $\alpha_n$  causes  $M$  to drop while current-dependent  $\alpha_p$  and  $\alpha_n$  rise as current increases. This causes forward bias across diode to fall off, giving rise to negative resistance region shown in (d).

Current continues to increase and voltage decreases until holes injected at anode of pnp equal the electrons injected at emitter of npn transistor. This condition results in saturation of the transistor model (forward-biased center junction of four-layer diode).



In reverse operating mode, four-layer diode or model appears as two reverse-biased diodes in series, passing small reverse current until breakdown occurs.

(Continued)
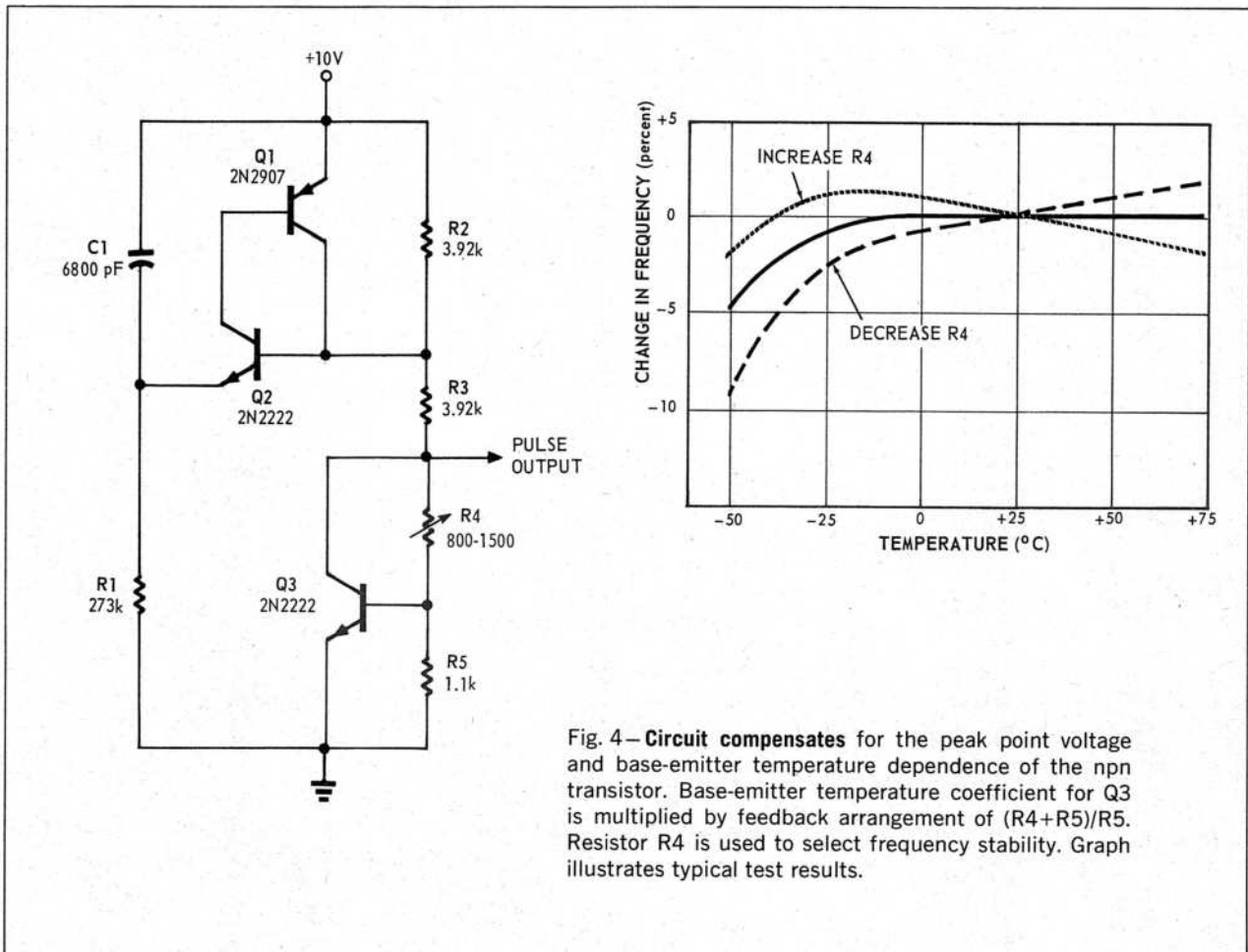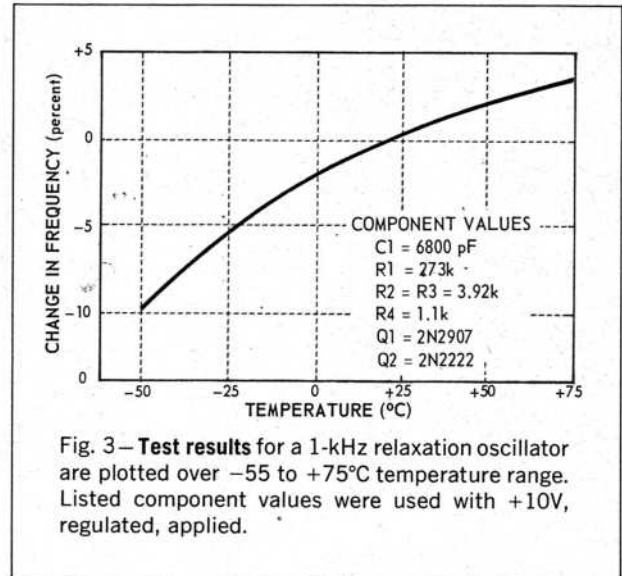
## Transistors (Cont'd)



results for the equivalent UJT oscillator would be altered by the temperature characteristics of R1 and C1. Frequency change for all graphs were normalized for 25°C and expressed as a percent change. Above 25°C, the frequency increases in an approximate linear manner and below 25°C, it decreases in a nonlinear manner. In fact, the frequency decreases as much as 10 percent at -50°C.

Accuracy depends on the repeatability of the peak point voltage. Metal film resistors with low temperature coefficients were used, but the  $V_{BE}$  drop varies approximately -1.5 to 2.0 mV/°C. Any major temperature dependence of the peak point voltage is because of npn base-emitter diode. Temperature stability also depends on the turn-off voltage or roughly the voltage that exists at the minimum holding current.




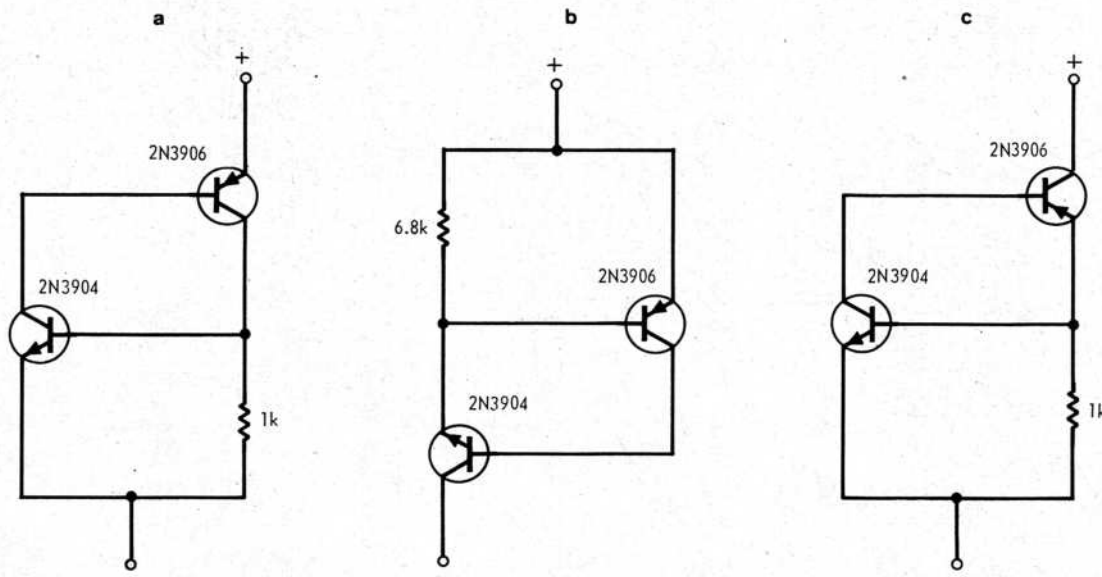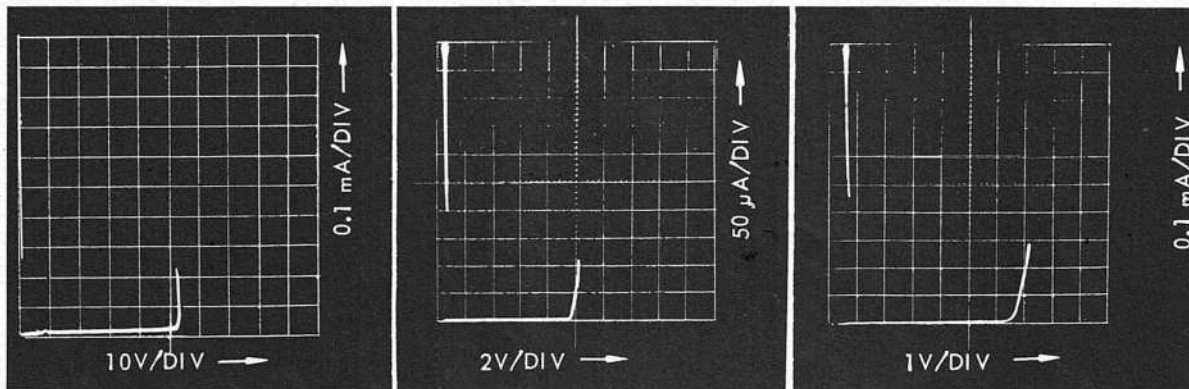
### THREE CONFIGURATIONS OF SIMULATED FOUR-LAYER DIODES



With the indicated connections, transistor current gain is much higher than that of four-layer diode. Breakover condition occurs at tenths of a volt. By shunting the emitter current path with a base-emitter resistor, very little injection takes place until the voltage across the shunt resistor begins to forward-bias the base-emitter junction. Shunt resistors can be placed across either pnp or npn transistor.

Forward V-I characteristics in (a) are for the circuit with the npn transistor shunted. Curves (a) and (c) are for two different 2N3906 transistors.  $BV_{ceo}$  is 55V (top), 65V (bottom).  $BV_{cer}$  of 2N3904 transistor is 120V. Breakover voltage of the pair is determined by the transistor with the lower breakdown parameter. Shunt resistors reduce base current gains and increase transistor breakdown voltage from  $BV_{ceo}$  to  $BV_{cer}$  "o" designating open, "r" representing a resistive shunt.

Breakover voltage below  $BV_{ceo}$  is attained by operating

either transistor in inverted mode, as in (b). Curve shows the result of inverting npn transistor, shunting base-emitter junction of pnp transistor. Even though  $\alpha$  for an inverted transistor is severely reduced, it is still necessary to reduce the  $\alpha$  of either the npn or pnp transistor with a shunt resistor. Here breakover voltage is determined by  $BV_{eco}$  of npn transistor, 10V. (A close approximation to breakover voltage is the more commonly specified  $BV_{ebo}$  voltage.)

A third four-layer diode equivalent is shown in (c), where the pnp transistor is inverted. Here the  $BV_{eco}$  voltage of pnp transistor determines the breakover point of the circuit, 6.5V.

Designers using proper transistor selection can synthesize four-layer diode breakover characteristics ranging from 5 to 100V or greater. Selecting suitable transistor current gains and shunt resistors, the holding current can be varied from a few  $\mu A$  to more than 20 mA.

(Continued)

## Transistors (Cont'd)

### Temperature Compensation

One method for compensating the peak point voltage and base-emitter temperature dependence is shown in Fig. 4. The  $V_{BE}$  temperature coefficient of Q3 is multiplied by the feedback arrangement of  $(R4 + R5)/R5$ . Optimum frequency stability over the temperature range of interest is established with the variable resistor R4. Typical test results are plotted on the graph (Fig. 4). Varying within a few tenths of a percent from 0 to 75°C, the frequency equals or exceeds the stability of the temperature-compensated p-base UJT. Over the -50 to +75°C temperature range, the frequency stability can be adjusted to approximately  $\pm 1.5$  percent—comparable to the n-base UJT oscillators.

Another approach, illustrated in Fig. 5 with test results, requires the addition of two diodes in the ground side of the biasing circuit. Since the compensation is scaled down by the voltage divider action of the biasing resistors, two diodes are necessary—thus, requiring one more  $V_{BE}$  characteristic to match. □

### Databank

Mr. Vincent recommends these references:

1. "The Unijunction Transistor and Its Applications", by T. P. Sylan, Publication No. 90.10, General Electric Co., Syracuse, N.Y., 1965. This report is considered the "classic" application note for the unijunction. Contains both theory and applications.
2. "Complementary Unijunction Transistor", by W. R. Spoford, Publication No. 90.72, General Electric Co., Syracuse, N.Y., 1968. Discusses GE's complementary unijunction transistor, which is a planar, monolithic integrated circuit.
3. "Unijunction Transistor Timers and Oscillators", App Note 294, Motorola Semiconductor Products, Phoenix, Ariz.



**Wes Vincent**, a graduate of the University of Iowa, is an electronic engineer with Motorola's Government Electronics Div., Space Systems Lab. This article is based in part upon his work toward a Master's degree at Arizona State University. In addition, Wes teaches electronics at Mesa Community College.

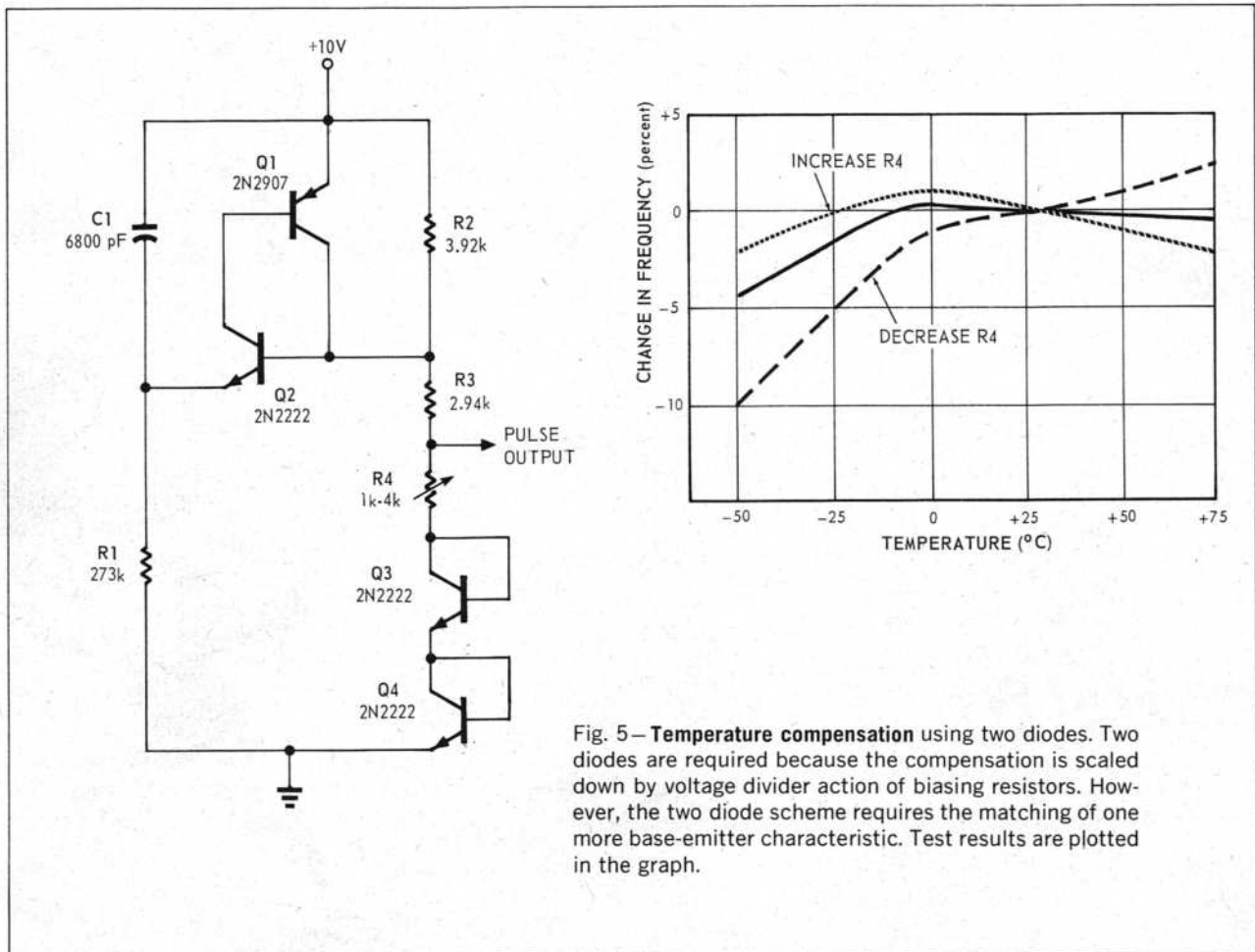


Fig. 5—Temperature compensation using two diodes. Two diodes are required because the compensation is scaled down by voltage divider action of biasing resistors. However, the two diode scheme requires the matching of one more base-emitter characteristic. Test results are plotted in the graph.

## Bipolar transistor pair simulates unijunction

by N.A. Shyne  
Montana State University, Bozeman, Mont.

The negative-resistance characteristic of a programmable unijunction transistor (PUT) can be simulated by interconnecting two discrete bipolar transistors. This equivalent PUT can not only switch faster than a conventional unijunction transistor, but it also offers better temperature stability. And parts cost can be as low as \$1.

The four-layer structure of a PUT is approximated by arranging complementary transistors  $Q_1$  and  $Q_2$  as shown in the figure. Applied bias voltage  $V$  tends to place the quiescent operating point of both transistors in their forward active regions. Current  $I$  is given by:

$$I = (I_{CO1} - I_{CO2}) / (1 - \alpha_{F1} - \alpha_{F2})$$

where  $\alpha_{F1}$  and  $\alpha_{F2}$  are the common-base short-circuit forward current gains of transistors  $Q_1$  and  $Q_2$ , respectively; and  $I_{CO1}$  and  $I_{CO2}$  are the respective reverse saturation currents of the base-collector junctions of  $Q_1$  and  $Q_2$ . (Current  $I_{CO1}$  is negative.)

In general, the numerator of this equation is not zero. As the sum of  $\alpha_{F1}$  and  $\alpha_{F2}$  approaches unity, current  $I$  increases without limit. The feedback between the two transistors is positive, since the collector current of  $Q_1$  is the base current of  $Q_2$ , and vice versa. The condition for regenerative feedback, then, is:

$$\alpha_{F1} + \alpha_{F2} = 1$$

or:

$$\beta_{F1} \beta_{F2} = 1$$

where  $\beta_{F1}$  and  $\beta_{F2}$  are the common-emitter short-circuit forward current gains of transistors  $Q_1$  and  $Q_2$ , respectively.

Resistors  $R_1$  and  $R_2$  permit the value of the equivalent PUT's intrinsic standoff ratio,  $\eta$ , to be varied. Let base B1 be the voltage reference point (ground), while base B2 is at a positive potential,  $V_{BB}$ . With the PUT's emitter (E) terminal open, the voltage at point B can then be expressed as:

$$V_B = [R_1 / (R_1 + R_2)] V_{BB} = \eta V_{BB}$$

so that:

$$\eta = R_1 / (R_1 + R_2)$$

If emitter voltage  $V_E$  is now increased to:

$$V_E = \eta V_{BB} + V_D$$


where  $V_D$  is the base-emitter voltage of transistor  $Q_1$ , both transistors will become saturated, and the PUT circuit will switch. When switching occurs, resistor  $R_1$  is shorted out by transistor  $Q_2$ , and:

$$V_{Emin} = V_D + V_{CE2sat}$$

where  $V_{CE2sat}$  is the collector-emitter saturation voltage of transistor  $Q_2$ . This value of  $V_{Emin}$  is usually lower than that of a conventional unijunction transistor. (Generally, it is best to use silicon transistors to keep leakage currents low so that the sum of  $\alpha_{F1}$  and  $\alpha_{F2}$  is less than unity with the PUT's emitter open.)

The switching speed of this equivalent PUT is limited only by the maximum operating frequency of the bipolar transistors used for  $Q_1$  and  $Q_2$ . Usually, the switching speed is considerably faster than that of a conventional unijunction transistor.

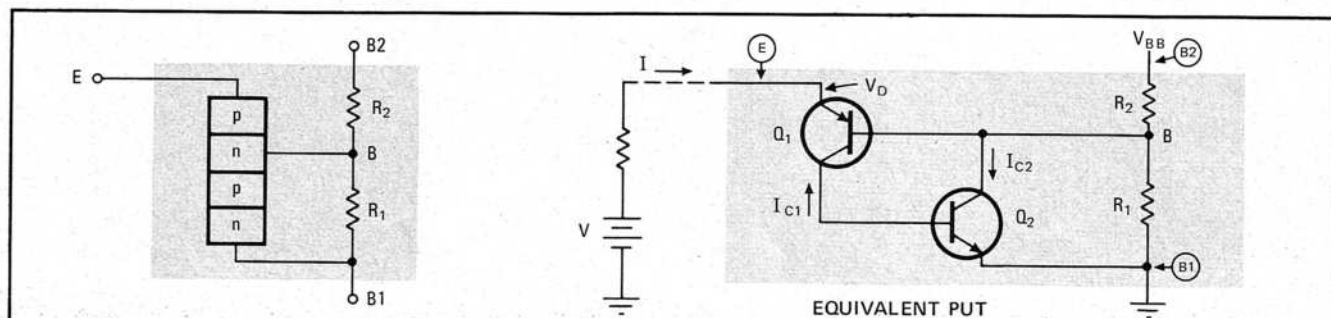If silicon transistors are used, the value of switching voltage  $V_D$  drifts only 3 millivolts/ $^{\circ}$ C. And with the proper selection of resistors  $R_1$  and  $R_2$ , intrinsic stand-



PERFORMANCE COMPARISON

PARAMETER	CONDITION	EQUIVALENT PUT*	TYPICAL UJT**
$R_{BB}$ , interbase resistance	$V_{BB} = 3 \text{ V}, I_E = 0$	9.4 k $\Omega$	6.2 - 9.1 k $\Omega$
$\eta$ , intrinsic standoff ratio	$V_{BB} = 10 \text{ V}$	0.5	0.51 - 0.62
$I_P$ , peak point current	$V_{BB} = 25 \text{ V}$	-160 nA	12 $\mu$ A max
$I_{EO}$ , emitter reverse current	25 $^{\circ}$ C	1 nA	2 $\mu$ A max
$I_V$ , valley current	$V_{BB} = 10 \text{ V}$	-200 $\mu$ A	8 mA

\*  $Q_1 = 2N4126, Q_2 = 2N4124, R_1 = R_2 = 4.7 \text{ k}\Omega$

\*\* UJT = 2N490A

**Simulating a unijunction transistor.** An equivalent programmable unijunction transistor (PUT) can be realized by wiring complementary bipolar transistors as shown. The resulting equivalent PUT offers faster switching and less temperature drift than an ordinary unijunction transistor (UJT). The table compares the major characteristics of the equivalent circuit to a typical UJT.



off ratio  $\eta$  can be made essentially independent of changing temperature.

The table compares the performance of the equivalent PUT to the performance of a typical unijunction

transistor, a type 2N490A device. For the comparison,  $R_1 = R_2 = 4.7$  kilohms and  $\epsilon = 0.5$ . A complementary (to the one shown) equivalent PUT can be made by just interchanging the positions of transistors  $Q_1$  and  $Q_2$ .  $\square$

## Program analyzes all-resistive dc circuits

by Mark Jong  
Wichita State University, Wichita, Kansas

Networks that are strictly resistive can be analyzed easily and quickly for dc conditions with a brief but effective computer program written in Basic. The circuit to be analyzed can also contain active devices, provided those devices can be represented by only resistive elements and voltage-dependent sources.


The standard circuit branch allowed by the program is shown in Fig. 1, along with the program listing. Nodes may be numbered in any order with consecutive integers beginning with zero. (The program always assumes that node 0 is the reference node.) Branches may also be numbered in any order with consecutive integers, but this set of numbers must begin with the number one.

The program first asks to know the number of nodes minus one, and then it requests the number of branches.

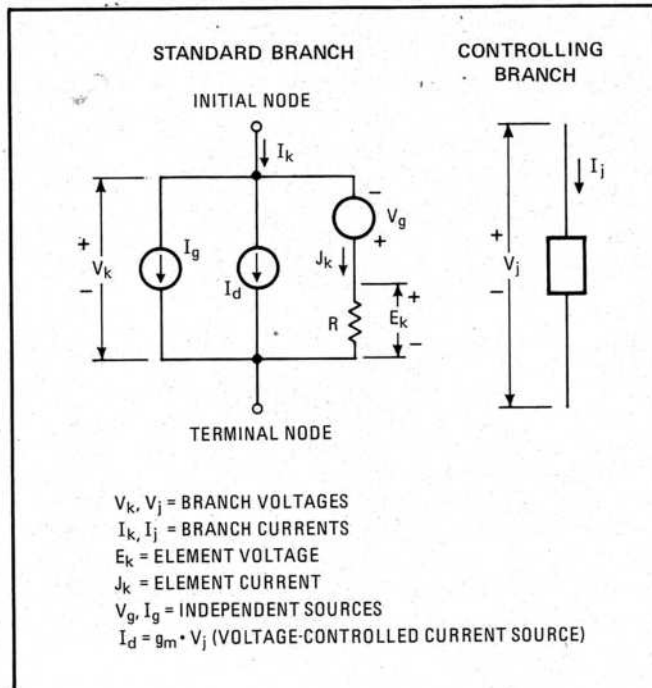**1. Dc circuit analysis.** Computer program, which is written in Basic, is useful for a speedy dc analysis of small resistive networks. The definitions for a standard circuit branch and the program listing itself are given here. Dependent sources must be voltage-controlled.

(A question mark is typed after each request.) The user responds by typing in the data requested each time, and pressing the RETURN key on his terminal.

After this preliminary input data is obtained, the program asks for the branch data by typing a question mark each time for each branch. In response, the user types in the data for each branch in a specific order and



```

100 DIM A(7,15),Y(15,15),E(15),I(15),
    J(15),V(15),S(15),W(15,7),U(15,7)
110 PRINT "NUMBER OF NODES - 1 = ";
111 INPUT N
120 PRINT "NUMBER OF BRANCHES = ";
121 INPUT B
130 MAT A=ZER(N,B)
140 MAT Y=ZER(B,B)
150 MAT E=ZER(B)
160 MAT I=ZER(B)
170 FOR K=1 TO B
180 INPUT B1,F1,T1,R,E(B1),I(B1),Y1,C1
190 IF F1=0 THEN 210
200 LET A(F1,B1)=1
210 IF T1=0 THEN 230
220 LET A(T1,B1)=-1
230 LET Y(B1,B1)=1/R
240 IF C1=0 THEN 260
250 LET Y(B1,C1)=Y1
260 NEXT K
270 MAT S=ZER(B)
275 MAT J=ZER(B)
280 FOR K=1 TO B
281 LET S(K)=Y(K,K)*E(K)
282 NEXT K
290 MAT S=I+S
295 MAT S=J-S
300 MAT W=ZER(B,N)
310 MAT W=TRN(A)
320 MAT U=ZER(B,N)
330 MAT U=Y*W
340 MAT W=ZER(N,N)
350 MAT W=A*U
360 MAT U=ZER(N,N)
370 MAT U=INV(W)
380 MAT V=ZER(N)
390 MAT V=A*S
400 MAT J=ZER(N)
410 MAT J=U*V
420 PPINT
430 PRINT "NODE"," VOLTAGE"
440 FOR K=1 TO N
450 PRINT K,J(K)
460 NEXT K
470 MAT V=ZER(B)
480 MAT W=ZER(B,N)
490 MAT W=TRN(A)
500 MAT V=W*J
510 MAT J=ZER(B)
520 MAT J=Y*V
530 MAT J=J-S
540 PPINT
550 PRINT "BRANCH"," VOLTAGE"," CURRENT"," POWER"
560 FOR K=1 TO B
570 PRINT K,V(K),J(K),V(K)*J(K)
580 NEXT K
590 MAT V=V+E
600 PRINT
610 PRINT "ELEMENT"," VOLTAGE"," CURRENT"," POWER"
620 FOR K=1 TO B
630 LET J(K)=Y(K,K)*V(K)
640 PRINT K,V(K),J(K),V(K)*J(K)
650 NEXT K
660 END

```



# replace one unijunction transistor


with  
two transistors

**Remember that circuit** you recently looked at and wanted to try? You passed on, though, right? The reason was quite simple. It used a unijunction transistor (UJT). Many hams have built up a collection of miscellaneous transistors in the junk box; the right combination to make your own UJT may be there waiting.

## the unijunction equivalent

The symbol for the unijunction is shown in **fig. 1A**. The two-transistor version of the UJT is shown in **fig. 1B**. The leads are labeled to correspond with **fig. 1A**. When the NPN and PNP transistors are connected as shown,

**fig. 1.** The schematic symbol for a UJT is shown in **A**. The equivalent two-transistor circuit is in **B**.

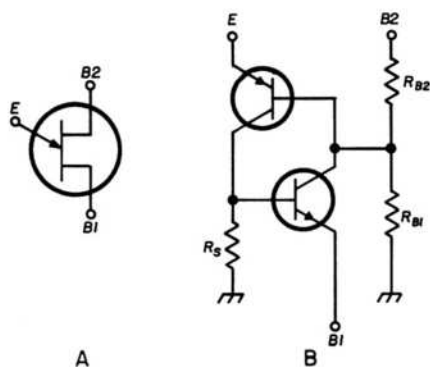

they effectively produce the equivalent internal construction of the UJT.

There is only one minor difference—it is necessary to add two resistors externally to

the circuit to produce the equivalent resistance found between each base lead and the emitter of the UJT. These two resistors are labeled  $R_{B1}$  and  $R_{B2}$  in the diagram. Resistor  $R_S$  is added for stability; a value around 10k should be sufficient.

As a general rule, the values of the two resistors  $R_{B1}$  and  $R_{B2}$  may be determined by knowing only two characteristics about the UJT you're replacing; the **intrinsic stand-off ratio** and the **interbase resistance**. These two characteristics are related by the formula:

$$\eta = \frac{R_{B1}}{R_{B1} + R_{B2}}$$

where  $\eta$  = intrinsic stand-off ratio

$R_{B1} + R_{B2}$  = equivalent interbase resistance


In unijunction transistors, the interbase resistance is typically between 5k and 10k ohms. The intrinsic standoff ratio of a common general-purpose UJT runs about 0.6. Using these values in the formula, you can quickly calculate that  $R_{B1}$  would have a value around 3k and  $R_{B2}$ , about 2k, to produce the equivalent of a general-purpose UJT.

In most applications, the actual values aren't critical and equal values of resistance could be used—such as 2.2k. This would produce an intrinsic stand-off ratio of 0.5 which is fine. If lower values of resistance are used, the circuit will draw more current and vice versa.

## unijunction code-practice oscillator

Now for an actual application. A code-practice oscillator using the two-transistor UJT equivalent is shown in fig. 2. Both tone and volume controls have been provided as well as a choice between speaker or ear-phones.

fig. 2. Here is a relatively simple CPO using the two-transistor equivalent UJT.

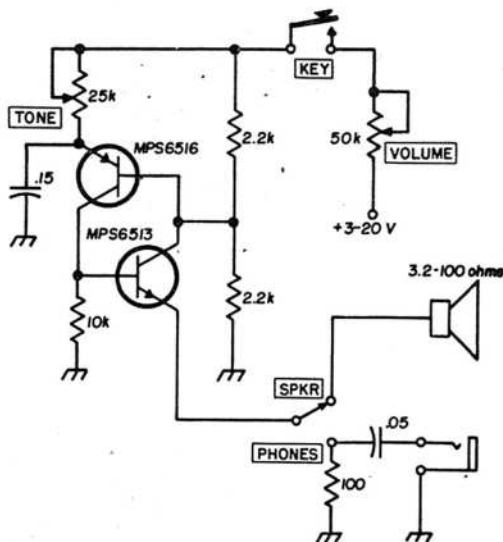

In this circuit, a 3-volt supply voltage was sufficient, but you can use as high as 20 volts. The actual voltage will depend upon your transistors and the output level you desire.

In general, a little experimenting with two transistors (one NPN and one PNP) will let you duplicate the function performed by the UJT—generally at lower cost. The transistors shown in fig. 2 are Motorola devices which are inexpensive and usable from audio through six meters: the latest price list shows the MPS 6513 at 57¢ and the MPS 6516 at 60¢. The price of these two transistors is in the ballpark of general-purpose UJT's, but with this approach, you may already have the UJT in your junk box.

Next time you start to bypass an article using a unijunction transistor, stop and think about how you could substitute two transistors and still have that same useful circuit.

### reference

General Electric Transistor Manual, Seventh Edition, 1964, page 300.

ham radio

## LOW PRICE, QUALITY, COAXIAL SWITCHES...



Don't pay for the 5th and 6th position. The average HAM rarely uses more than 4!

SPECIFICATIONS: Silvered Contacts. Write-on ERASABLE escutcheon plate. AVAILABLE EITHER 4 PST (COAX-4) OR LINEAR (COAX-LINEAR) IN-OUT VERSION. Handles 1000 W AM or 2000 W SSB. Insertion loss negligible to 160 Mc. VSWR: Less than 1.2 at 160 Mc. Size: 3 5/8" dia. x 1 5/8" overall. Single hole mount. SPECIFY MODEL. \$7.65 ea.

## COAXIAL LIGHTNING ARRESTORS



Zero power loss. No increase in SWR at 150 Mc. Does not attenuate signals. Model 210 for 1000 W (AM) or 2000 W (SSB). Model 211 Electronic static arrester for 50 W (AM) or 100 W (SSB). SO-239 UHF type fittings. Other fittings available. Size approx. 3 1/2" x 3/4" dia. #210 \$3.15 ea. #211 \$4.65 ea. SPECIFY model #.

PRICES above are amateur net. Shipped ppd. in U.S.A. Send Check or M.O. (N.J. ADD 3% Sales Tax)

OTHER PRODUCTS: Feed thru capacitors. Tuned noise filters. Alternator, generator, low-pass and field filters. SEND FOR CATALOG.

**"COMMUNICATION ENGINEERED"**  
By "HAMMIE" RICHARDT—W2W1Y

**ELECTRONIC APPLICATIONS CO.**  
ROUTE 46, Pine Brook, N. J. 07058

Interested in saving money?  
Turn to page 47

## oscillator/monitor

- a sensitive broadband RF detector gives audible tone signal in the presence of any RF field from 10mw to 1 kw and 100kc to 1000mc
- a CW monitor with positive "RF" switch uses only 8" pickup antenna and NO connection to rig or key
- a code practice oscillator with adjustable tone & built in speaker
- high gain 4 transistor circuit powered by long life AA pencil
- 16 gauge aluminum cabinet in white & black epoxy finish, 3 1/2" by 2 3/8" by 1 1/4", weight 8 ounces
- 100% US made and guaranteed



**1295** (batt incl)  
ppd usa & can  
send cert ck or m.o.  
ny res add 5% tax

the James research company  
11 schermerhorn st., brooklyn n.y. 11201